

## ME242 – MECHANICAL ENGINEERING SYSTEMS

### LECTURE 25:

- Intermediate Modeling – Simple Circuits 4.1

## INTERMEDIATE MODELING

*Start second pass of modeling process*

- Bond graphs with many bonds and junctions
- Include multiple transformers and gyrators
- More bond graph reduction, model equivalences

## SIMPLE CIRCUITS

Creation of simple multi-element bond graphs

### Key Concepts:

- Each element has two sides
- Elements interconnect by simple junctions
- Graph simplified by removal of ground
- Remove two ported multiports

### Slight Differences:

- Electrical and Fluid very similar
- Mechanical slightly different


## ELECTRIC CIRCUITS

Identify all nodes and all elements  
(*there are two nodes for each element*)


1. Represent each **electrical junction (node)** with a 0 junction
  - Represent each element with I, R or C  
(*each element gets a bond to it*)
2. Connect each element's bond to a 1 junction
  - Connect each 1 junction to 2 0 junctions
3. Discard all bonds for  $e = 0$  (ground) and  $i = 0$
4. Eliminate all junctions with only two bonds

## ELECTRIC CIRCUITS


Example:

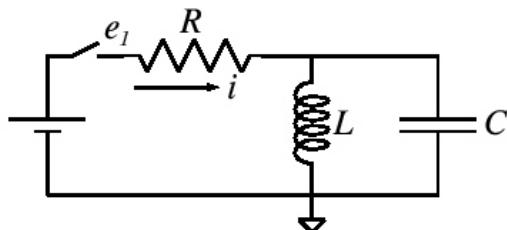


Identify elements and nodes

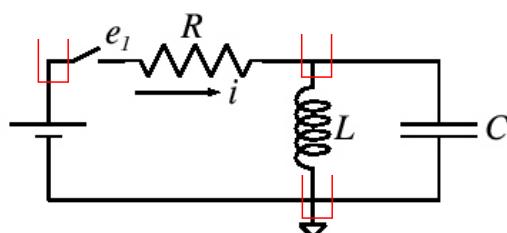


## ELECTRIC CIRCUITS

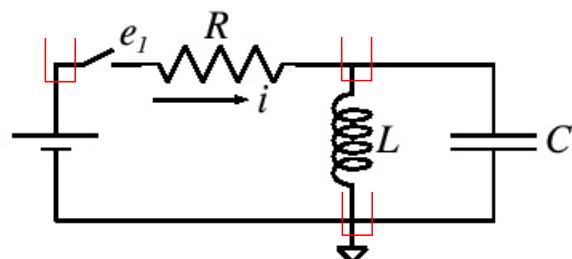


Add junctions

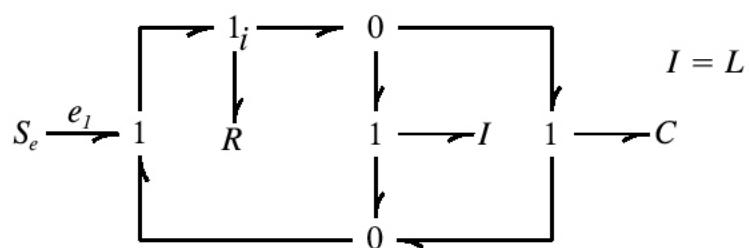


## ELECTRIC CIRCUITS

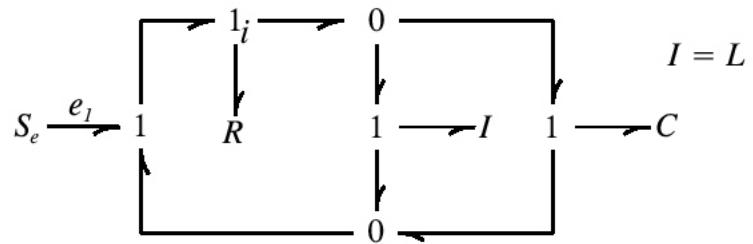

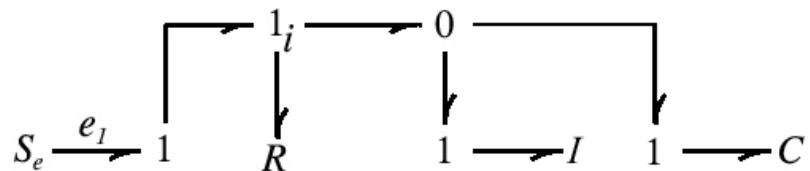
Remove  $e = 0, i = 0$  bonds  $\Downarrow$



## ELECTRIC CIRCUITS

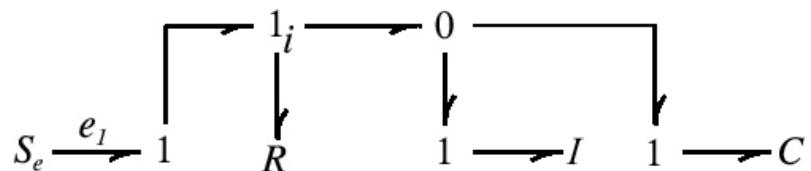

Remove 2 ported multiports  $\Downarrow$

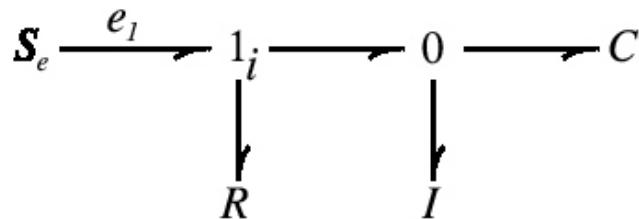

With practice can draw final graph in one step.

## ELECTRIC CIRCUITS

Identify all nodes and all elements  
(*there are two nodes for each element*)

1. Represent each **electrical junction (node)** with a 0 junction
  - Represent each element with I, R or C  
(*each element gets a bond to it*)
2. Connect each element's bond to a 1 junction
  - Connect each 1 junction to 2 0 junctions
3. Discard all bonds for  $e = 0$  (ground) and  $i = 0$
4. Eliminate all junctions with only two bonds

## FLUID CIRCUITS


Identify all nodes and all elements  
(*there are two nodes for each element*)

1. Represent each node with a 0 junction
  - Represent each element with I, R or C  
(*each element gets a bond to it*)
2. Connect each element's bond to a 1 junction
  - Connect each 1 junction to 2 0 junctions
3. Discard all bonds for  $e = 0$  (ground) and  $i = 0$
4. Eliminate all junctions with only two bonds


Just like  
electrical  
circuits!

## FLUID CIRCUITS



Example:

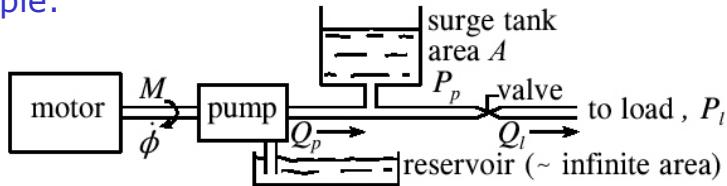

Identify elements and nodes

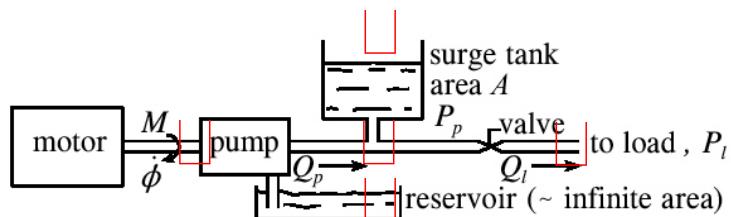

## FLUID CIRCUITS

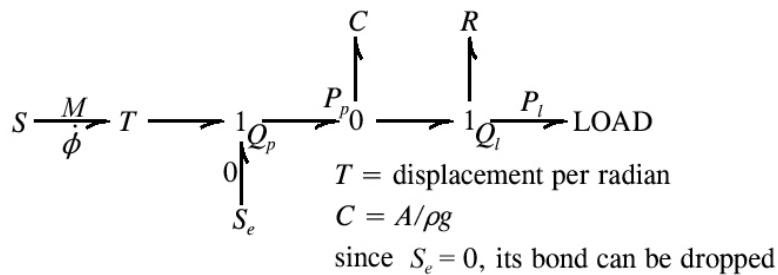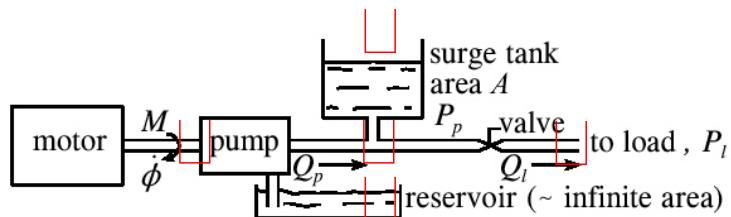


## MECHANICAL CIRCUITS

Identify all nodes and all elements  
(there are two nodes for each element)


1. Represent each mech. junction with a 1 junction  
□ Place all I's on 1 junctions
2. Connect each R, C elements on a 0 junction  
□ Connect each 0 junction to 2 1 junctions
3. Coalesce bonded junctions of same type
4. Add in S,  $S_e$   $S_f$  as needed.
5. Discard all bonds for  $e = 0$  (ground) and  $f = 0$
6. Eliminate all junctions with only two bonds

## MECHANICAL CIRCUITS


Example:

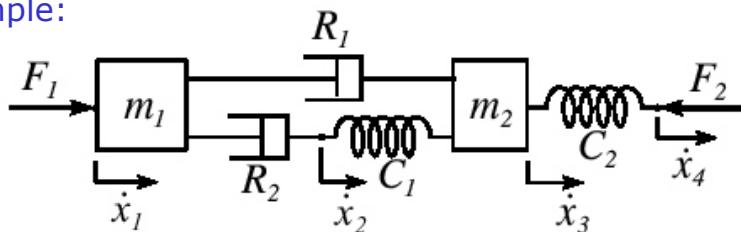


Identify elements and junctions

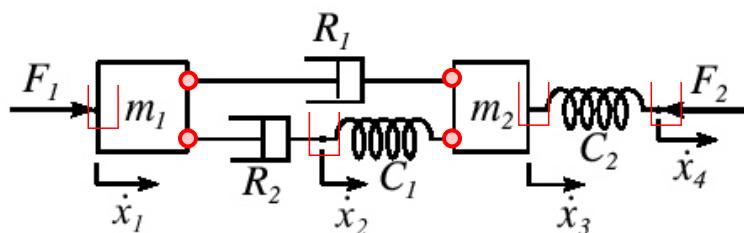


## MECHANICAL CIRCUITS

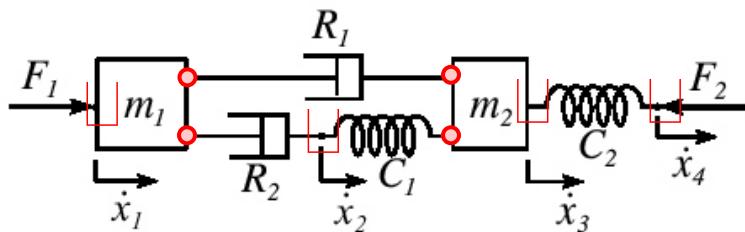

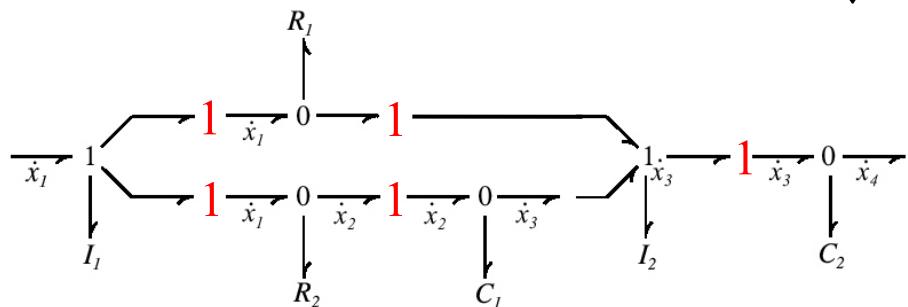I's to 1's, C's and R's to 0 and 1's for junctions  $\Downarrow$



## MECHANICAL CIRCUITS

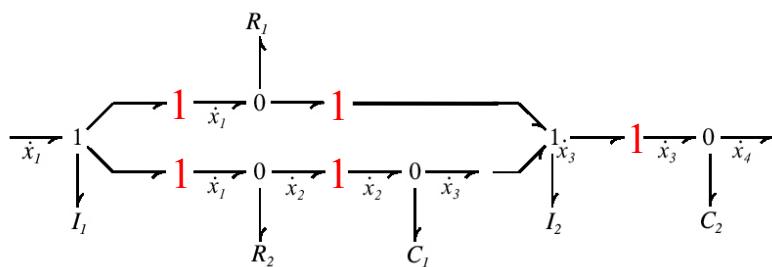

Delete bonds for  $e=0$ ,  $f=0$ , 2 ported multports, add S's  $\Downarrow$

